



Dr. D. Y. Patil Unitech Society

DR. D. Y. PATIL INSTITUTE OF TECHNOLOGY

(formerly Dr. D. Y. Patil Institute of Engineering and Technology)

Sant Tukaram Nagar, Pimpri, Pune.

DEPARTMENT OF ELECTRONICS & TELECOMMUNICATION

Electrical Circuit Virtual Lab

Savitribai Phule Pune University

Second Year of E & TC Engineering (2019 Course)

204187: Electrical Circuits Lab




EXPERIMENT 1

To verify Kirchhoff's Laws: Kirchhoff's Current Law, Kirchhoff's Voltage Law

Procedure

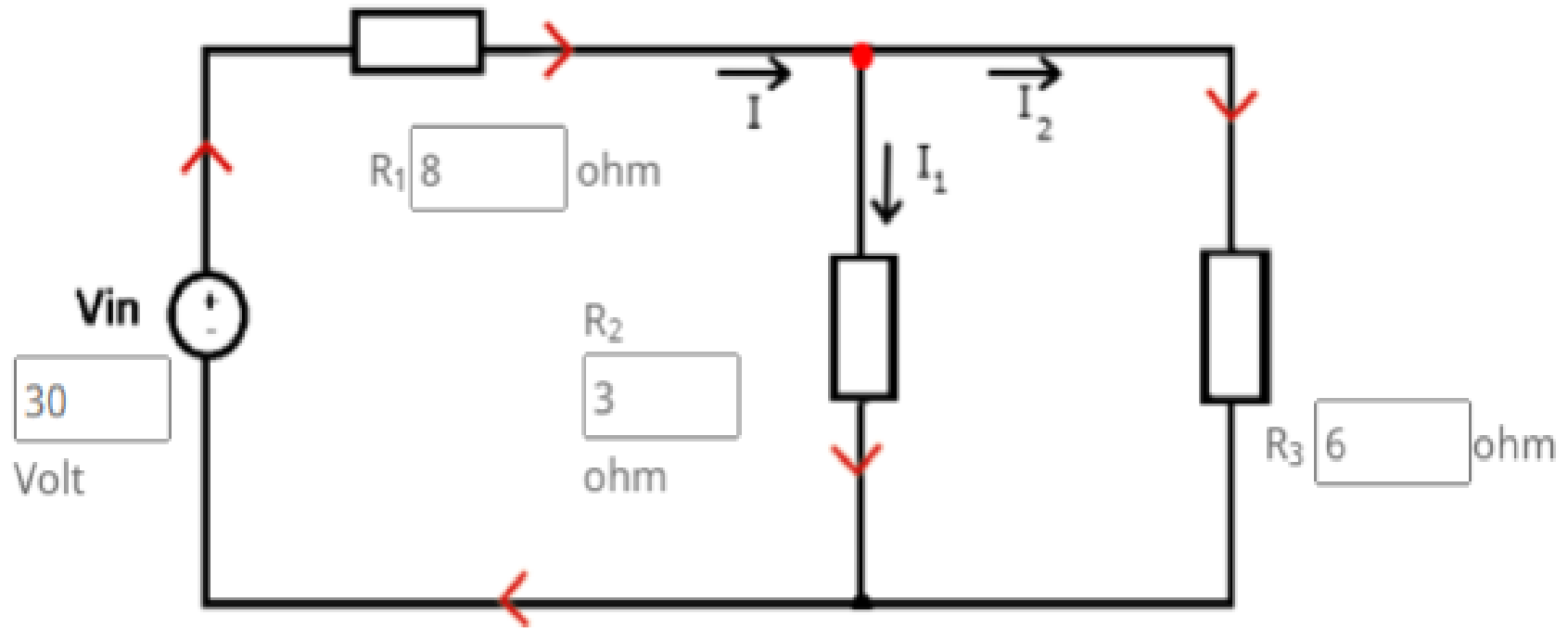- 1) Set the values of Resistors(R_1, R_2, R_3) and battery (V_{in}).
(range for battery voltage is:1V to 300V and Resistors : 1 ohm to 10k ohm)



2) Put the values in Kirchhoff's equations given. **Solve the equations to find voltage ,current ,power in each resistor.**

Equations:

$$1) \quad I_1(R_1+R_2)+R_1I_2 = V_{in}$$

$$2) \quad R_3I_2-R_2I_1 = 0$$

$$3) \quad I=I_1+I_2$$

$$4) \quad P=V.I$$

3) Put the values which you have calculated in tabular form as shown.

	Voltage(in volt)	Current(in amp)	Power(in watt)
R1	24	3	72
R2	6	2	12
R3	6	1	6

4) Click on **Verify Voltage** ,**Verify Current** ,**Verify Power** buttons to verify your answers.

	Voltage(in volt)	Current(in amp)	Power(in watt)
R1	24	3	72
R2	6	2	12
R3	6	1	6

Verify Voltage

Verify Current

Verify Power

Voltage Verified.

Current Verified.

Power Verified.

5) Click on the **Click here to see answer button** to see correct answers if you want. Answers will be displayed in the table.

[Click here to see answer](#)

	Voltage (in volt)	Current(in amp)	Power(in watt)
R1	24.00	3.00	72.00
R2	6.00	2.00	12.00
R3	6.00	1.00	6.00