



Dr. D. Y. Patil Unitech Society

**DR. D. Y. PATIL INSTITUTE OF TECHNOLOGY**

(formerly Dr. D. Y. Patil Institute of Engineering and Technology)

Sant Tukaram Nagar, Pimpri, Pune.

DEPARTMENT OF ELECTRONICS & TELECOMMUNICATION

# **Electrical Circuit Virtual Lab**

**Savitribai Phule Pune University**

**Second Year of E & TC Engineering (2019 Course)**

**204187: Electrical Circuits Lab**




## EXPERIMENT 3

To study the Load Characteristics of DC shunt generator


# Procedure:

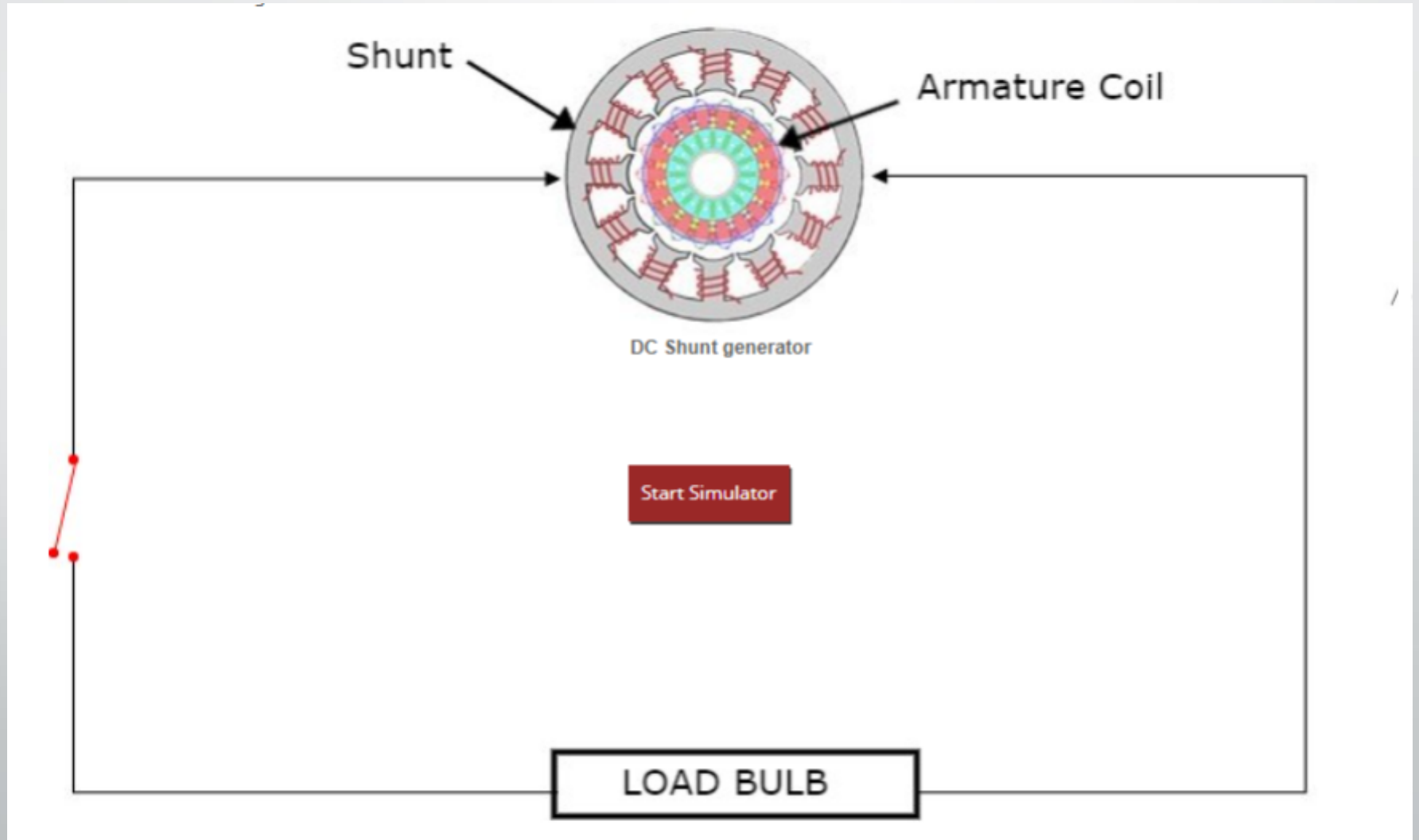- 1) Go to the Simulator tab and click on **Start Simulator**.




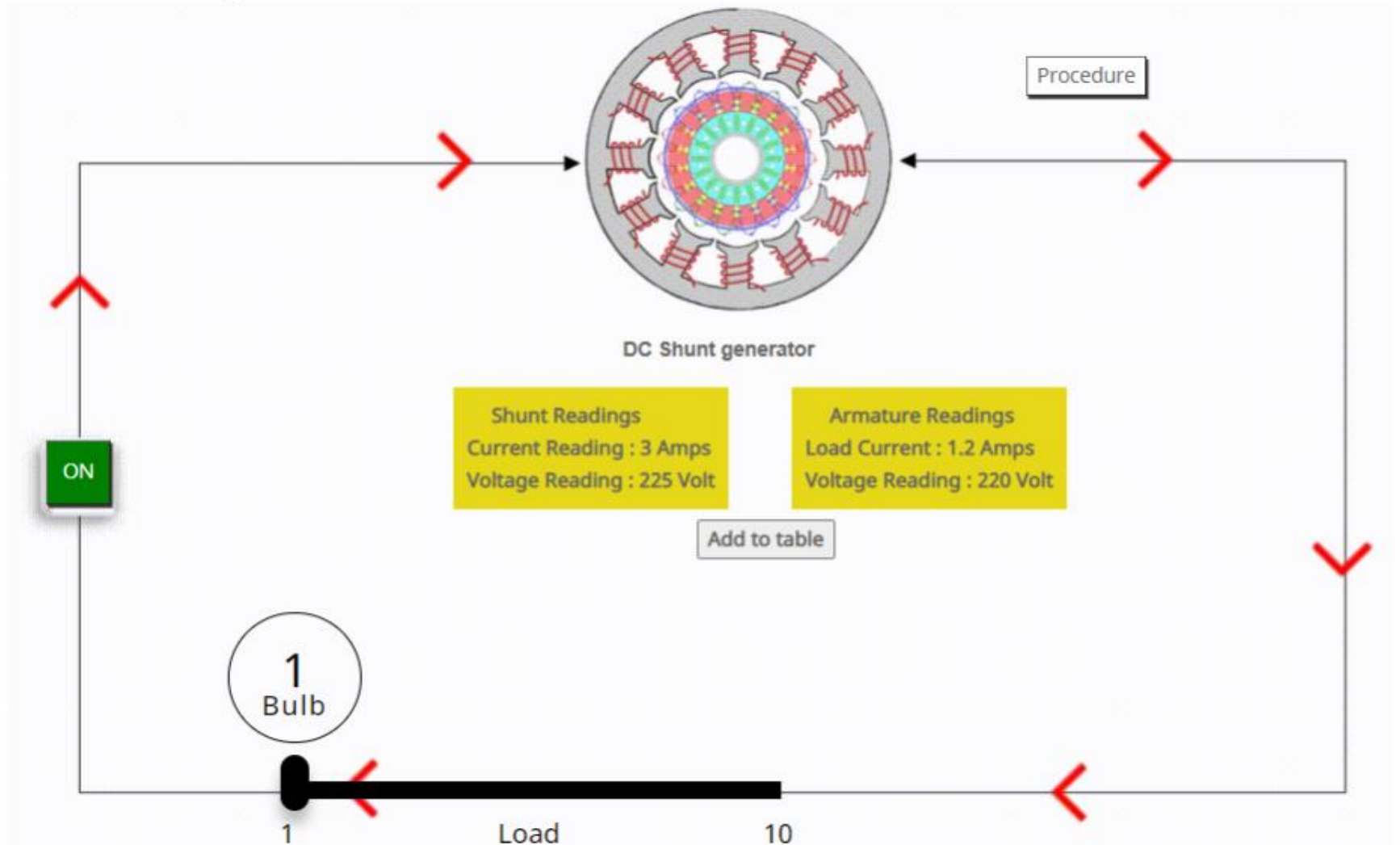2) Note the shunt and armature readings for current and voltage when the load is of 1 bulb. Click on **Add to table** button to save the readings.


Study the Load Characteristics of DC shunt generator > Simulator



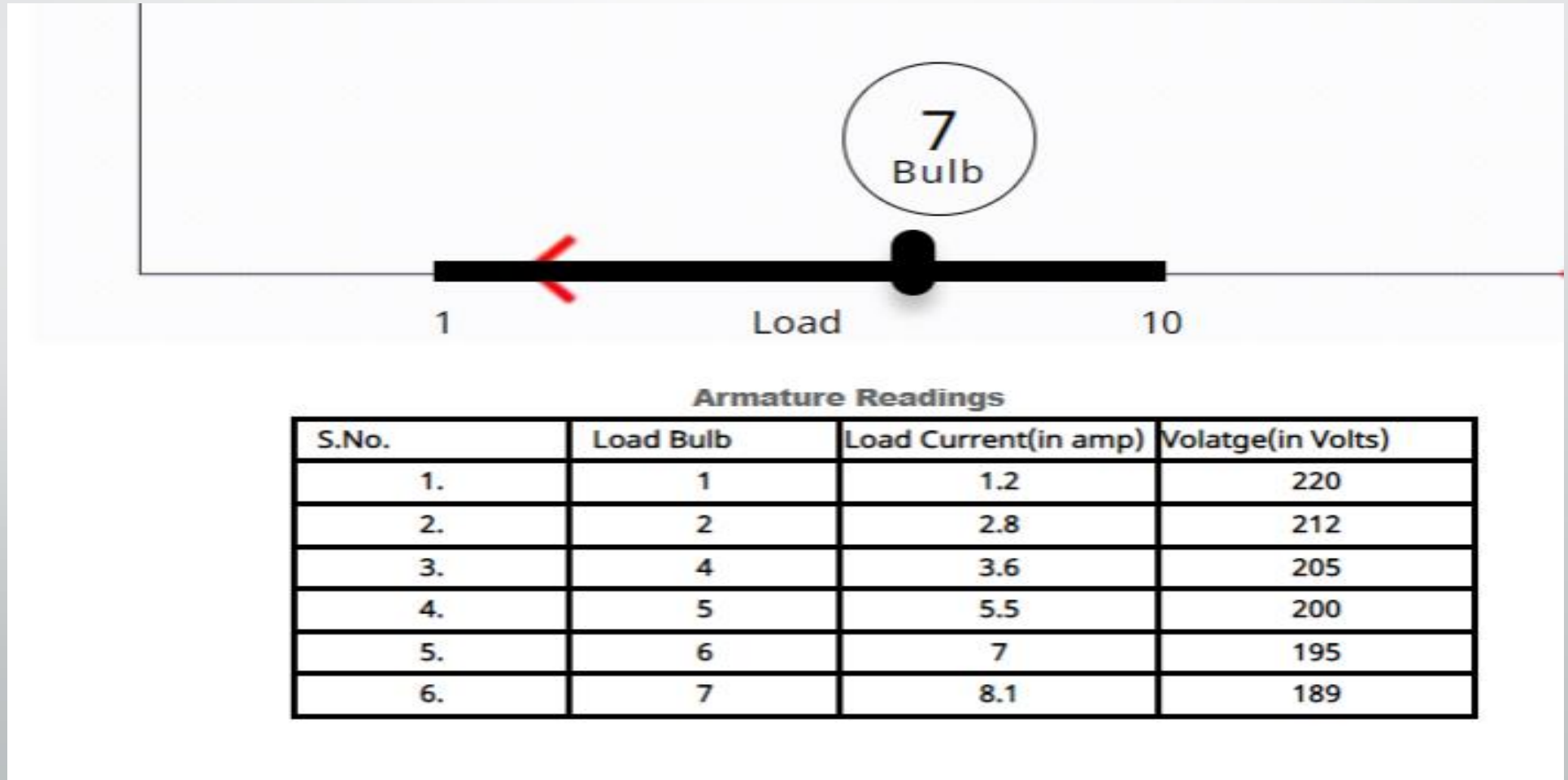3) Now, increase the number of bulbs i.e. load gradually and observe the change in current and voltage. Also click on the **Add to table** button for each increment. Maximum 6 readings are possible.



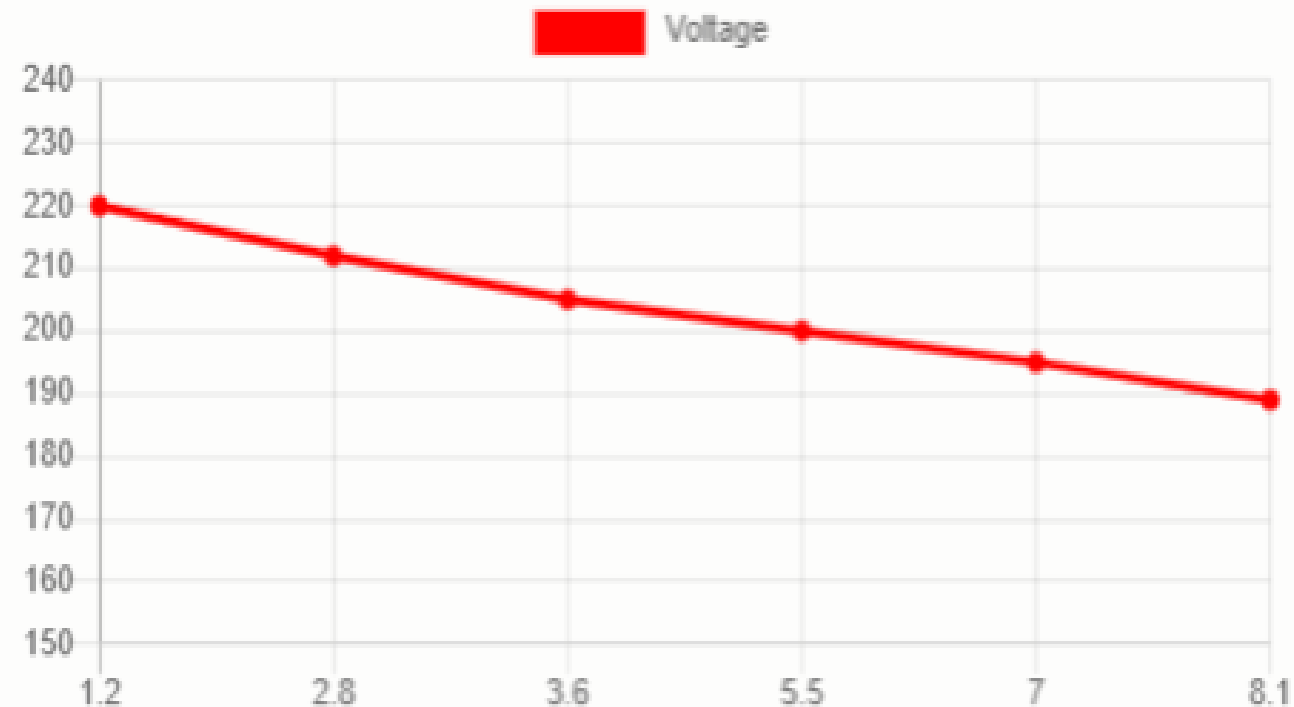4) Click on Plot Graph button. Load characteristics of DC generator will be displayed according to the values in the table. Observe the relation between load current and terminal voltage.



Graph Shows that whenever Load Current Increases Voltage Decreases.

5) Click on **Reset** button to reset all the values and to take the new set of readings.

**Armature Readings**

S.No.	Load Bulb	Load Current(in amp)	Volatge(in Volts)
1.			
2.			
3.			
4.			
5.			
6.			

Reset

Plot Graph

