



Dr. D. Y. Patil Unitech Society

DR. D. Y. PATIL INSTITUTE OF TECHNOLOGY

(formerly Dr. D. Y. Patil Institute of Engineering and Technology)

Sant Tukaram Nagar, Pimpri, Pune.

DEPARTMENT OF ELECTRONICS & TELECOMMUNICATION

Electrical Circuit Virtual Lab

Savitribai Phule Pune University

Second Year of E & TC Engineering (2019 Course)

204187: Electrical Circuits Lab



EXPERIMENT 1

To verify Kirchhoff's Laws: Kirchhoff's Current Law, Kirchhoff's Voltage Law



AIM : To verify the Kirchhoff's voltage law and Kirchhoff's current law for the given circuit.



OBJECTIVE


- To measure voltage and current in a DC circuit for each element.
- To calculate analytically V and I .
- Compare analytical and practical values.
- Verify KCL and KVL.
- To apply concepts of KCL and KVL in network theorems.

THEORY


Basic Laws of Electric Circuits

□ Nodes and Branches:

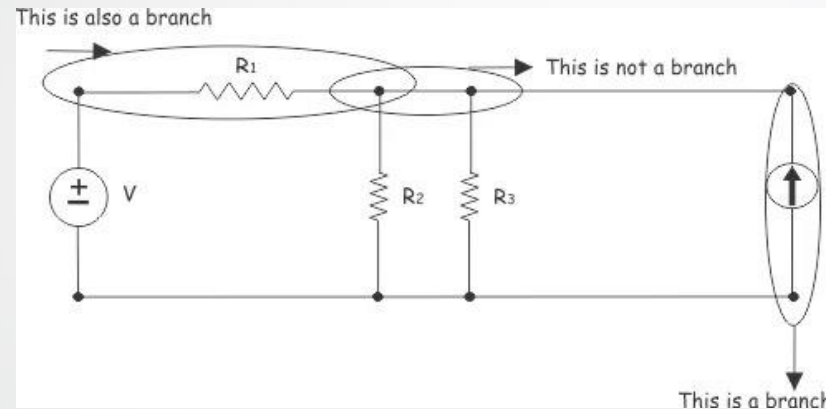- ✓ A branch: A branch is a single electrical element or device.




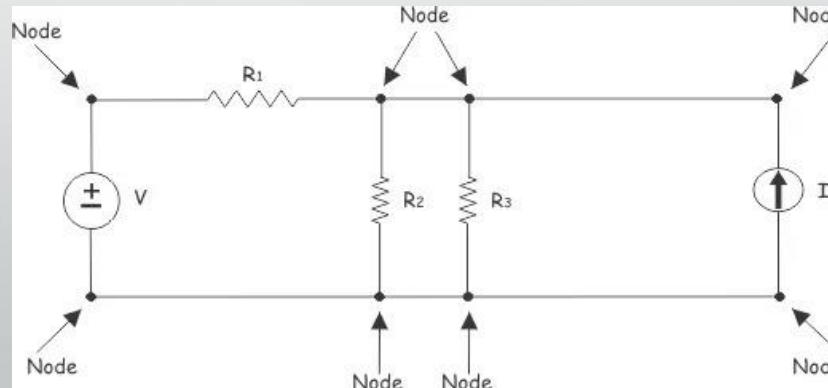- ✓ A node: A node can be defined as a connection point between two or more branches.




Kirchhoff's Current Law

- ❑ **Kirchhoff's Current Law or KCL**, states that the *"total current or charge entering a junction or node is exactly equal to the charge leaving the node as it has no other place to go except to leave, as no charge is lost within the node"*.
- ❑ In other words the algebraic sum of ALL the currents entering and leaving a node must be equal to zero, $I_{(\text{exiting})} + I_{(\text{entering})} = 0$.
- ❑ This idea by Kirchhoff is commonly known as the **Conservation of Charge**.

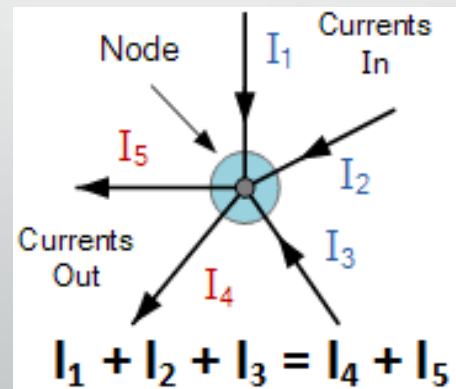


Kirchhoff's Voltage Law

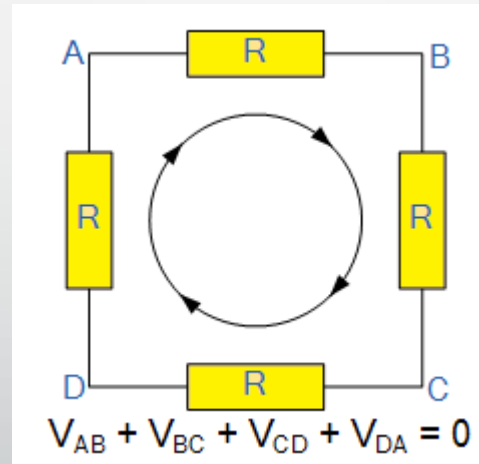- ❑ **Kirchhoff's Voltage Law or KVL**, states that *"in any closed loop network, the total voltage around the loop is equal to the sum of all the voltage drops within the same loop"* which is also equal to zero.
- ❑ In other words the algebraic sum of all voltages within the loop must be equal to zero.
- ❑ This idea by Kirchhoff is known as the **Conservation of Energy**.



Kirchhoff's Rules

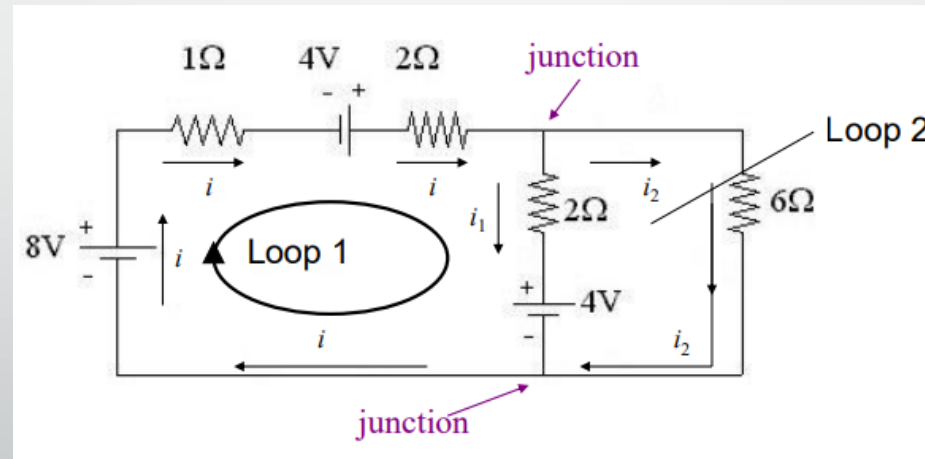- Many practical resistor networks cannot be reduced to simple series-parallel combinations (see an example below).
- Terminology:
 - A junction in a circuit is a point where three or more conductors meet.
 - A loop is any closed conducting path.







Kirchhoff's Rules

- ❑ **Junction Rule:** The sum of the magnitudes of the currents directed into a junction equals the sum of the magnitudes of the currents directed out of the junction.
- ❑ **Loop Rule:** Around any closed circuit loop, the sum of the changes in potential around any closed path of a circuit must be zero.

Kirchhoff's Rules

- ❑ **Kirchhoff's junction rule:** The algebraic sum of the currents into any junction is zero.

$$\sum I = 0 \text{ at any junction}$$

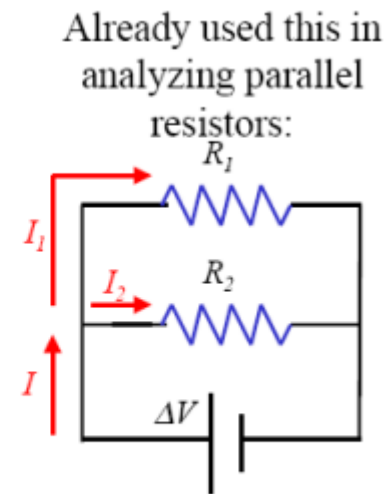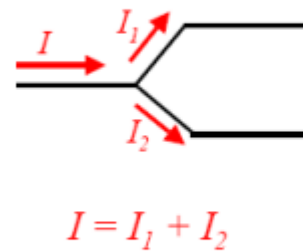


Kirchhoff's Rules

- ❑ **Kirchhoff's Loop Rule:** The algebraic sum of the potential differences in any loop, including those associated with emfs and those of resistive elements, must equal zero.

$$\sum V=0 \text{ at any Loop}$$

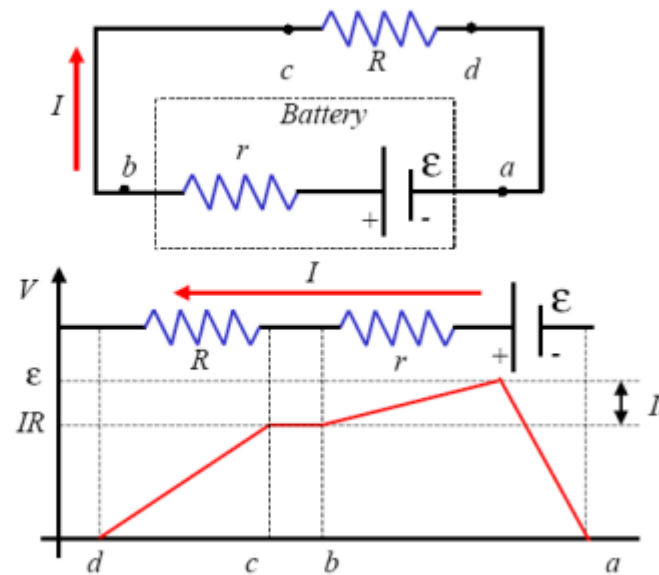Already used this
in analyzing series
resistors:







Kirchhoff's Rules

❑ Rules for Kirchhoff's loop rule:

- ✓ When a resistor is traversed in the same direction as the current, the change in potential is $-IR$.
- ✓ When a resistor is traversed in the direction opposite to the current, the change in potential is $+IR$.
- ✓ When an emf is traversed from $-$ to $+$ (the same direction it moves positive charge), the change in potential is $+emf$.
- ✓ When an emf is traversed from $+$ to $-$ (opposite to the direction it moves positive charge), the change in potential is $-emf$.

Kirchhoff's Rules


Rules for Kirchhoff's loop rule

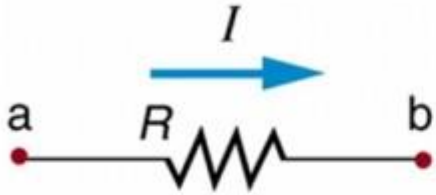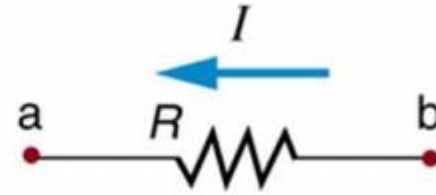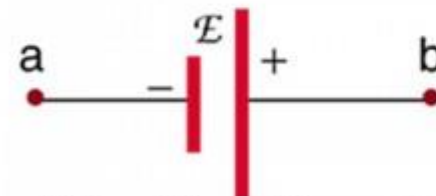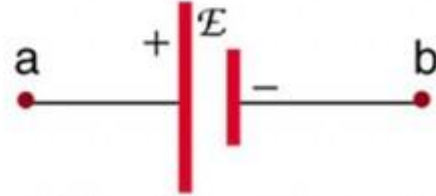Direction of traverse a \longrightarrow b	Direction of traverse a \longrightarrow b
	
$\Delta V = V_b - V_a = -IR$	$\Delta V = V_b - V_a = +IR$
Direction of traverse a \longrightarrow b	Direction of traverse a \longrightarrow b
	
$\Delta V = V_b - V_a = +\mathcal{E}$	$\Delta V = V_b - V_a = -\mathcal{E}$

Kirchhoff's Rules

□ Example 1

Find currents I_1 , I_2 , and I_3 .

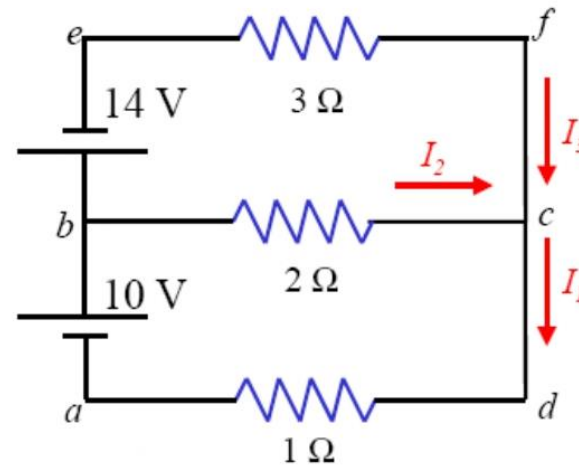

1. Apply the junction rule at c .

$$I_2 + I_3 = I_1$$

2. Apply the loop rule in the **clockwise** direction for loop $abcda$.


$$10\text{ V} - (2\Omega)I_2 - (1\Omega)I_1 = 0$$

3. Apply the loop rule in the **clockwise** direction for loop $befcb$.

$$-14\text{ V} - (3\Omega)I_3 + (2\Omega)I_2 = 0$$

Kirchhoff's Rules

□ Example 1 (cont' d)

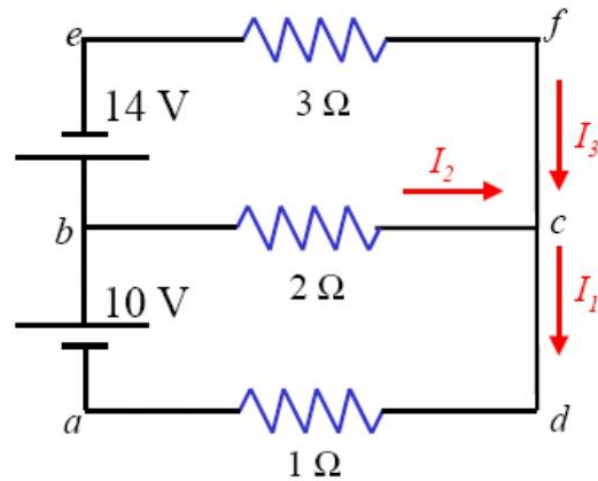

$$\textcircled{1} \quad I_1 = I_2 + I_3$$

$$\textcircled{2} \quad 10 \text{ V} - (2\Omega)I_2 - (1\Omega)I_1 = 0$$

$$\textcircled{3} \quad -14 \text{ V} - (3\Omega)I_3 + (2\Omega)I_2 = 0$$

Substituting $\textcircled{1}$ into $\textcircled{2}$ gives

$$10 - 2I_2 - (I_2 + I_3) = 0$$


$$\textcircled{4} \quad 10 = 3I_2 + I_3$$

Rearranging $\textcircled{3}$ gives

$$\textcircled{5} \quad 14 = 2I_2 - 3I_3$$

Kirchhoff's Rules

□ Example 1 (cont' d)

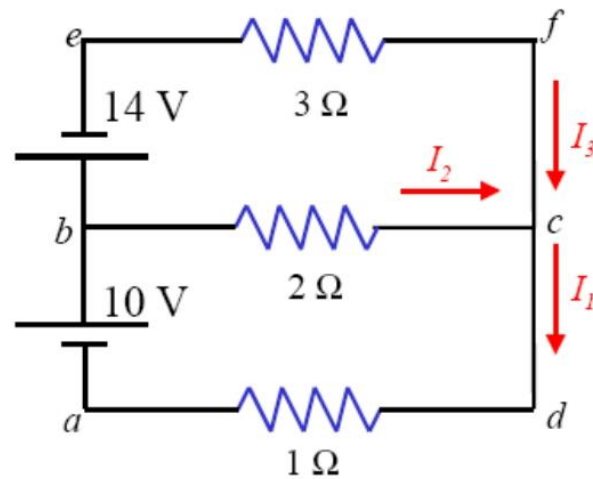

$$\textcircled{1} \quad I_1 = I_2 + I_3$$

$$\textcircled{4} \quad 10 = 3I_2 + I_3$$

$$\textcircled{5} \quad 14 = 2I_2 - 3I_3$$

Multiplying $\textcircled{4}$ by 3 and adding to $\textcircled{5}$ gives

$$44 = 11I_2$$

$$I_2 = 4\text{A}$$

Using this in $\textcircled{5}$ gives

$$I_3 = -2\text{A}$$

Finally $\textcircled{1}$ gives

$$I_1 = 2\text{A}$$