



Dr. D. Y. Patil Unitech Society

**DR. D. Y. PATIL INSTITUTE OF TECHNOLOGY**

(formerly Dr. D. Y. Patil Institute of Engineering and Technology)

Sant Tukaram Nagar, Pimpri, Pune.

DEPARTMENT OF ELECTRONICS & TELECOMMUNICATION

## **Electrical Circuit Virtual Lab**

**Savitribai Phule Pune University**

**Second Year of E & TC Engineering (2019 Course)**

**204187: Electrical Circuits Lab**



## EXPERIMENT 2

To study and verify Parallel RC & RL Circuit




## OBJECTIVE


- To design parallel RC circuit and find out the current flowing through each component.
- To design parallel RL circuit and find out the current flowing through each component.

# THEORY

## Parallel RC Circuit

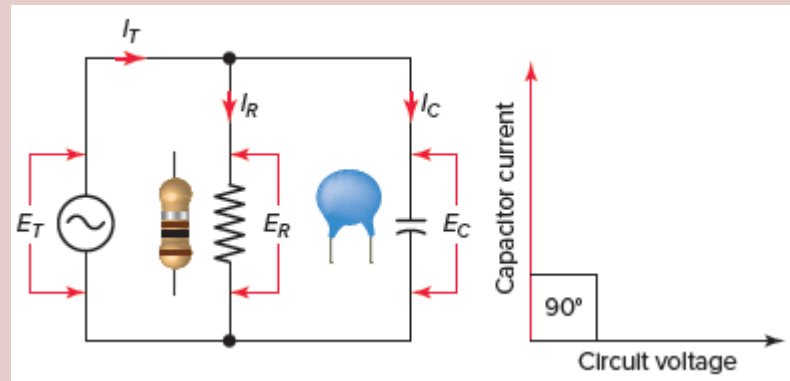


Parallel RC Circuit

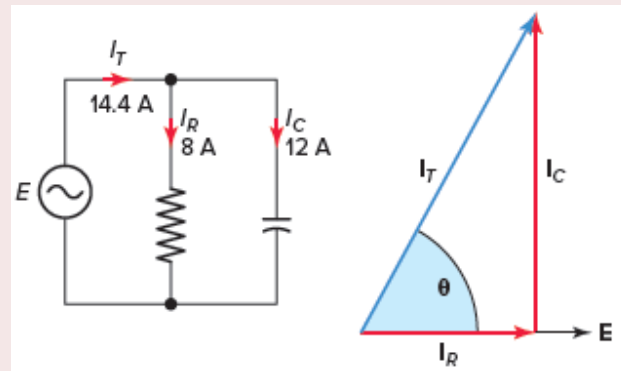


Parallel RC Circuit Phasor Vector Diagram

$$\theta = \tan^{-1} \frac{I_C}{I_R}$$

## Parallel RL Circuit

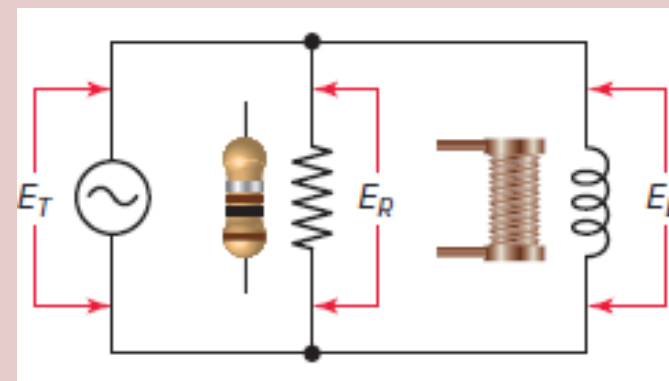

Parallel RL Circuit

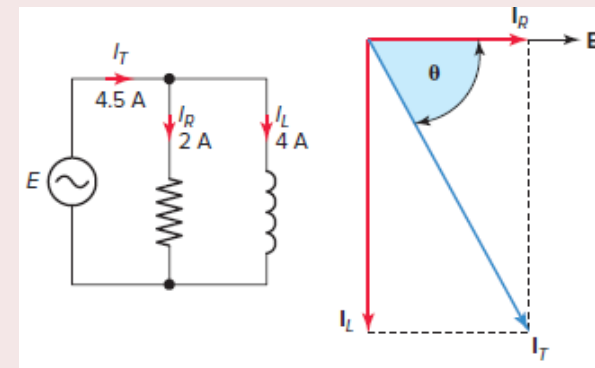

Parallel RL Circuit Phasor Vector Diagram


$$\theta = \tan^{-1} \frac{I_L}{I_R}$$

# THEORY

## Parallel RC Circuit

$$Z = \frac{RX_c}{\sqrt{R^2 + X_c^2}}$$

Impedance

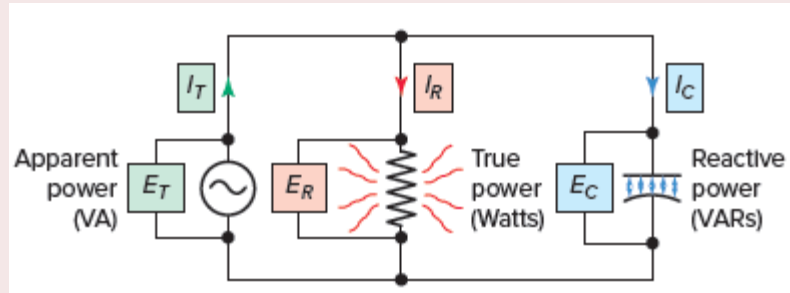

Power components of a RC parallel circuit


$$\text{Power factor} = \frac{I_R}{I_T}$$

$$\text{Power factor} = \frac{Z}{R}$$

## Parallel RL Circuit

$$Z = \frac{RX_L}{\sqrt{R^2 + X_L^2}}$$

Impedance

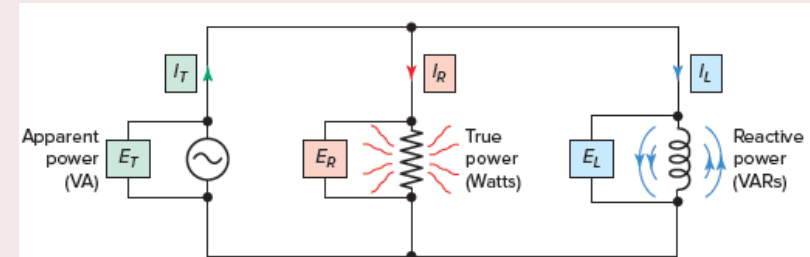

Power components of a RL parallel circuit

$$\text{Power factor} = \frac{I_R}{I_T}$$

$$\text{Power factor} = \frac{Z}{R}$$

# THEORY

## Parallel RC Circuit

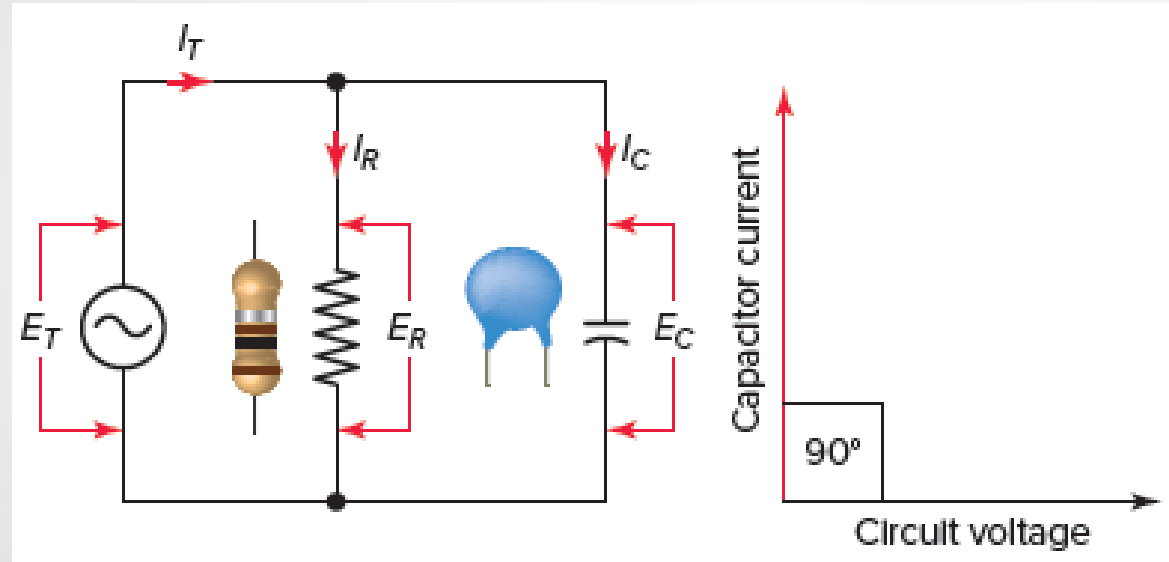


Figure 1 : Parallel RC circuit

## Parallel RC Circuit Phasor Diagram

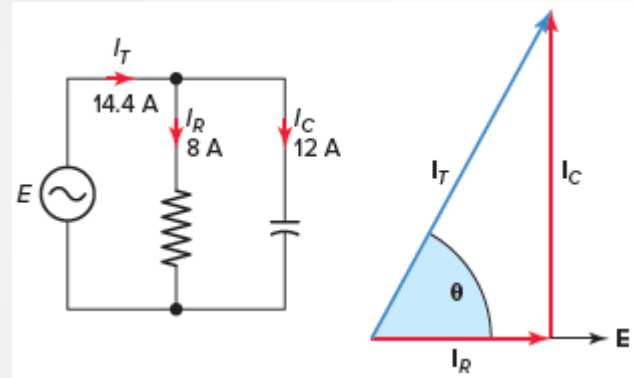


Figure 2 : Parallel RC circuit  
vector (phasor) diagram

## Parallel RC Circuit Phasor Diagram

The relationship between the voltage and currents in a parallel RC circuit is illustrated in the vector (phasor) diagram of Figure 2 and summarized as follows:

- The ***reference vector is labeled  $E$***  and represents the voltage in the circuit, which is common to all elements.
- Since the current through the resistor is in phase with the voltage across it,  $I_R$  (8 A) is shown superimposed on the voltage vector.
- The capacitor current  $I_C$  (12 A) leads the voltage by 90 degrees and is positioned in an upward direction, leading the voltage vector by 90 degrees.



## Parallel RC Circuit Phasor Diagram

The relationship between the voltage and currents in a parallel RC circuit is illustrated in the vector (phasor) diagram of Figure 2 and summarized as follows:

- The ***reference vector is labeled  $E$***  and represents the voltage in the circuit, which is common to all elements.
- Since the current through the resistor is in phase with the voltage across it,  $I_R$  (8 A) is shown superimposed on the voltage vector.
- The capacitor current  $I_C$  (12 A) leads the voltage by 90 degrees and is positioned in an upward direction, leading the voltage vector by 90 degrees.

## Parallel RC Circuit Phasor Diagram

- The vector addition of  $I_R$  and  $I_C$  gives a resultant that represents the total ( $I_T$ ) or line current (14.4 A).

$$\begin{aligned} I_T &= \sqrt{I_R^2 + I_C^2} \\ &= \sqrt{8^2 + 12^2} \\ &= \sqrt{208} \\ &= 14.4 \text{ A} \end{aligned}$$

- The angle theta ( $\theta$ ) represents the phase between the applied line voltage and current.

## Parallel RC Circuit Phasor Diagram

In a parallel RC circuit, the ***line current leads the applied voltage*** by some phase angle less than 90 degrees but greater than 0 degrees. The exact angle depends on whether the capacitive current or resistive current is greater. If ***there is more capacitive current, the angle will be closer to 90 degrees***, while if the resistive current is greater, the angle is closer to 0 degrees.

The value of the phase angle can be calculated from the values of the two branch currents using the following equation:

$$\theta = \tan^{-1} \frac{I_C}{I_R}$$

# THEORY

## Parallel RL Circuit

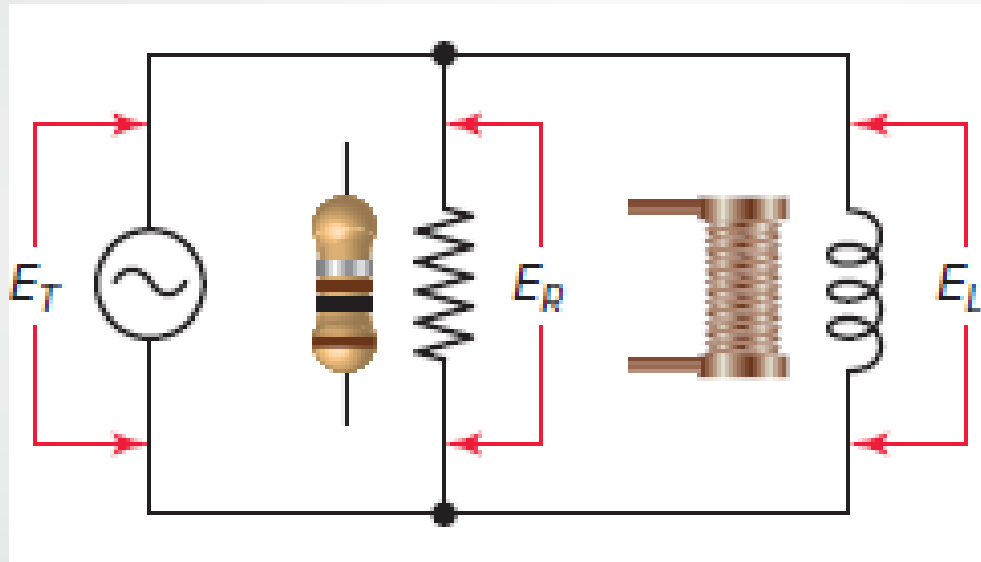


Figure 1 : Parallel RL circuit

## Parallel RC Circuit

The combination of a resistor and inductor connected in parallel to an AC source, as illustrated in Figure 1, is called a ***parallel RL circuit***. In a parallel DC circuit, the voltage across each of the parallel branches is equal. This is also true of the **AC *parallel circuit***.

The voltages across each parallel branch are:

- The same value.
- Equal in value to the total applied voltage  $E_T$ .
- All in phase with each other.

Therefore, for a RL parallel circuit

$$E_T = E_R = E_L$$

## Parallel RL Circuit Phasor Diagram

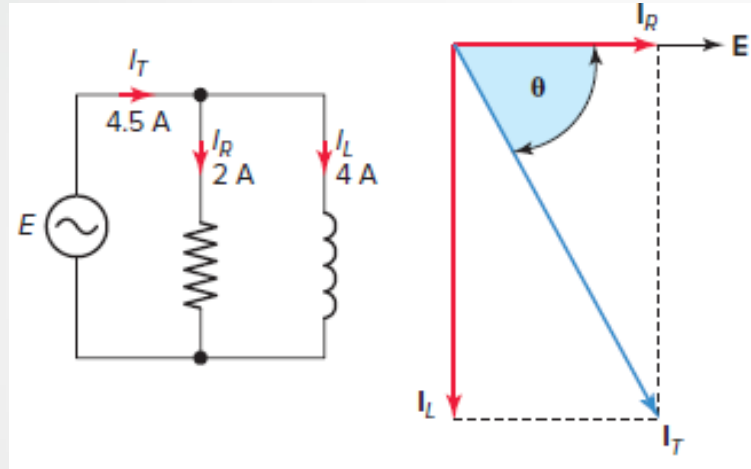


Figure 2 : Parallel RL circuit  
vector (phasor) diagram

## Parallel RL Circuit Phasor Diagram

The relationship between the voltage and currents in a parallel RL circuit is illustrated in the vector (phasor) diagram of Figure 2 and summarized as follows:

- The ***reference vector is labeled  $E$***  and represents the voltage in the circuit, which is common to all elements.
- Since the current through the resistor is in phase with the voltage across it,  $I_R$  (2 A) is shown superimposed on the voltage vector.
- The inductor current  $I_L$  (4 A) lags the voltage by 90 degrees and is positioned in a downward direction lagging the voltage vector by 90 degrees.
- The vector addition of  $I_R$  and  $I_L$  gives a resultant that represents the total ( $I_T$ ), or line current (4.5 A).
- The **angle theta ( $\theta$ )** represents the phase between the applied line voltage and current.

## Parallel RL Circuit Phasor Diagram

As is the case in all parallel circuits, the current in each branch of a parallel RL circuit acts **independent** of the currents in the other branches. The current flow in each branch is determined by the voltage across that branch and the opposition to current flow, in the form of either resistance or inductive reactance, contained in the branch.

**Ohm's law** can then be used to find the individual branch currents as follows:

$$I_R = \frac{E}{R}$$
$$I_L = \frac{E}{X_L}$$



## Parallel RL Circuit Phasor Diagram

The resistive branch current has the same phase as the applied voltage, but **the inductive branch current lags the applied voltage by 90 degrees**. As a result, the total line current ( $I_T$ ) consists of  $I_R$  and  $I_L$  90 degrees out of phase with each other.

The current flow through the resistor and the inductor form the legs of a right triangle, and the total current is the hypotenuse. Therefore, the Pythagorean theorem can be applied to add these currents together by using the equation:

$$I_T = \sqrt{I_R^2 + I_L^2}$$

## Parallel RL Circuit Phasor Diagram

In all parallel RL circuits, the phase angle theta ( $\theta$ ) by which the total current lags the voltage is somewhere between 0 and 90 degrees. The size of the angle is determined by whether there is **more inductive current or resistive current**.

If there is more inductive current, the phase angle will be closer to 90 degrees. It will be closer to 0 degrees if there is more resistive current. From the circuit vector diagram you can see that the value of the phase angle can be calculated from the equation:

$$\theta = \tan^{-1} \frac{I_L}{I_R}$$